



CSE 205: DIGITAL LOGIC DESIGN


Dr. Tanzima Hashem

Associate Professor

CSE, BUET

PROGRAMMABLE LOGIC ARRAYS (PLAs)

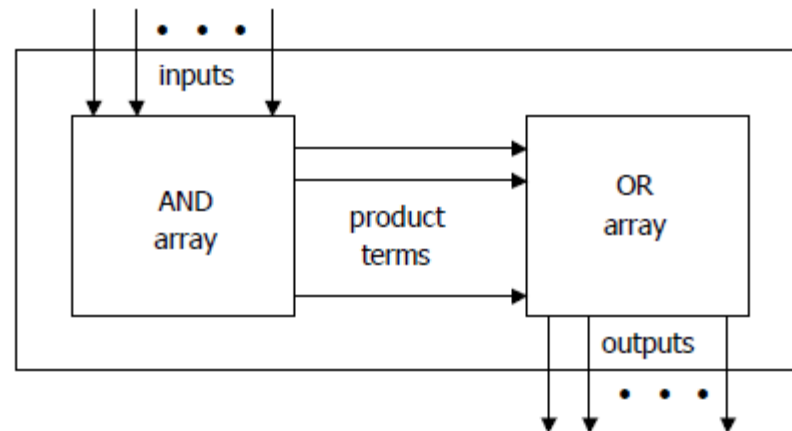- Pre-fabricated building block of many AND/OR gates




- An array of programmable AND gates
 - can generate any product terms of the inputs
- An array of programmable OR gates
 - can generate the sums of the products



PROGRAMMABLE LOGIC ARRAYS (PLAs)

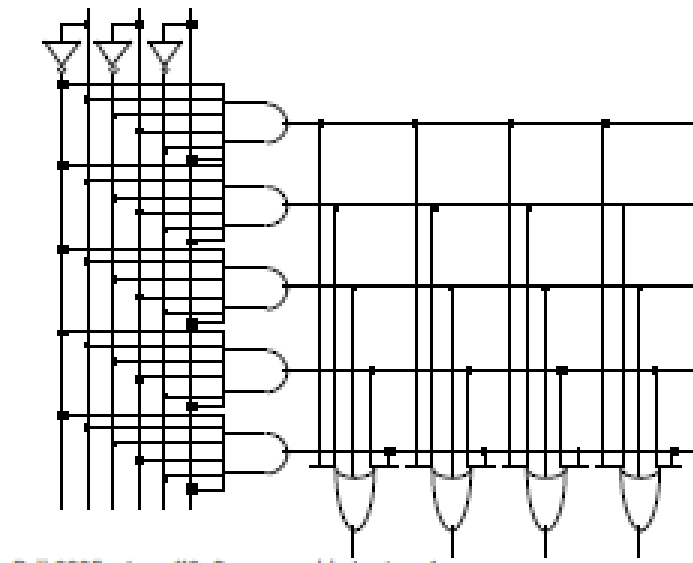- Before programming, all possible connections available before "programming"
- "Personalized" by making or breaking connections among gates



PLA EXAMPLE

- Example: AND/OR/XOR
 - $F1 = AB' + AC + A'BC'$
 - $F2 = (AC + BC)'$
- XOR gates can invert the outputs
 - invert: connected to 1
 - not change: connected to 0
- PLA programming table: 3 sections
 1. list the product terms
 2. specify the required paths between inputs and AND gates
 3. specify the paths between the AND and OR gates

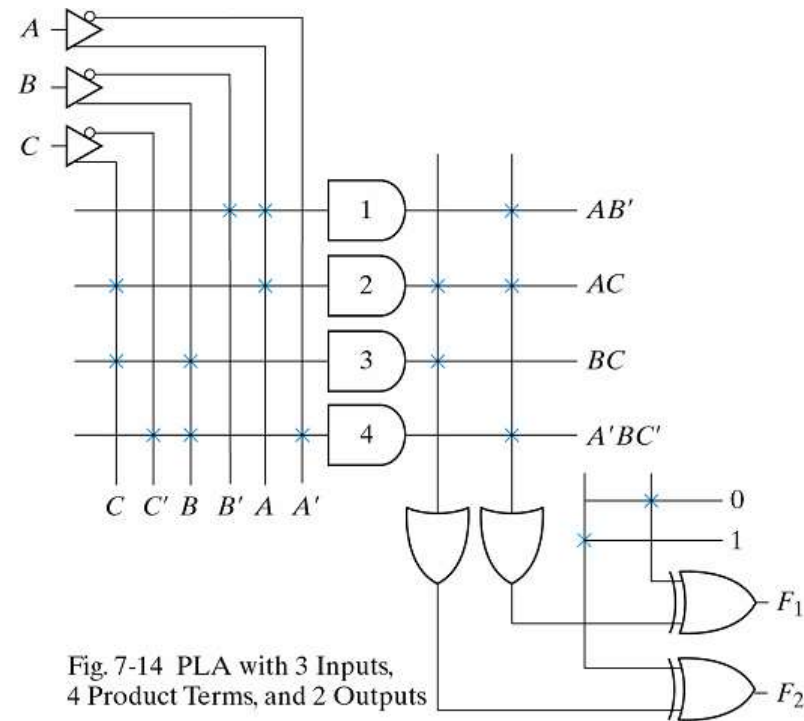


Fig. 7-14 PLA with 3 Inputs, 4 Product Terms, and 2 Outputs

Table 7-5 PLA Programming Table

Product Term		Inputs			Outputs (T) (C)	
		A	B	C	F ₁	F ₂
AB'	1	1	0	—	1	—
AC	2	1	—	1	1	1
BC	3	—	1	1	—	1
A'BC'	4	0	1	0	1	—

PROGRAMMABLE LOGIC ARRAYS (PLAs)

- Size of PLA: specified by # of inputs, product terms and outputs
 - n inputs, k product terms and m outputs
 - n buffer-inverter gates, k AND gates, m OR gates, and m XOR gates
- Designing a digital system with a PLA
 - reduce the number of distinct product terms
 - the number of literals in a product is not important



IMPLEMENT WITH PLAS

- $F_1(A, B, C) = \Sigma (0, 1, 2, 4)$;
 $F_2(A, B, C) = \Sigma (0, 5, 6, 7)$
- Simply both the true and complement of the functions in sum of products
- Find the combination with minimum number of product terms
 - $F_1 = (AB + AC + BC)'$
 - $F_2 = AB + AC + A'B'C'$
- Obtain the PLA programming table

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	1	0	1
	1	1	0	0	0

$$F_1 = A'B' + A'C' + B'C'$$

$$F_1 = (AB + AC + BC)'$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	0	0	0
	1	0	1	1	1

$$F_2 = AB + AC + A'B'C'$$

$$F_2 = (A'C + A'B + AB'C')'$$

PLA programming table

	Product term	Outputs				
		Inputs			(C)	(T)
		<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i> ₁	<i>F</i> ₂
<i>AB</i>	1	1	1	–	1	1
<i>AC</i>	2	1	–	1	1	1
<i>BC</i>	3	–	1	1	1	–
<i>A'B'C'</i>	4	0	0	0	–	1

Fig. 7-15 Solution to Example 7-2



SYLLABUS

- Chapter 7:7.6

